

Connections
AREF VCC
ADXL 335-
VCC - VCC
GND-GND
X_OUT-A0
Y_OUT-A1
Z_OUT-A2
LED 1,2,3 GND-GND
LED 1,2,3-8,9,10 port no


Important Note
For ADXL 335
AREF in Arduino must
be connected to VCC
port

ADXL 335 has three
axis measurment. But
in coading only Z axis
is used. You can put all
connection or keep
only z axis connection
that is A2

Here Top line is ground

Black wire is GND
Blue is VCC

Here Bottom line is
ground

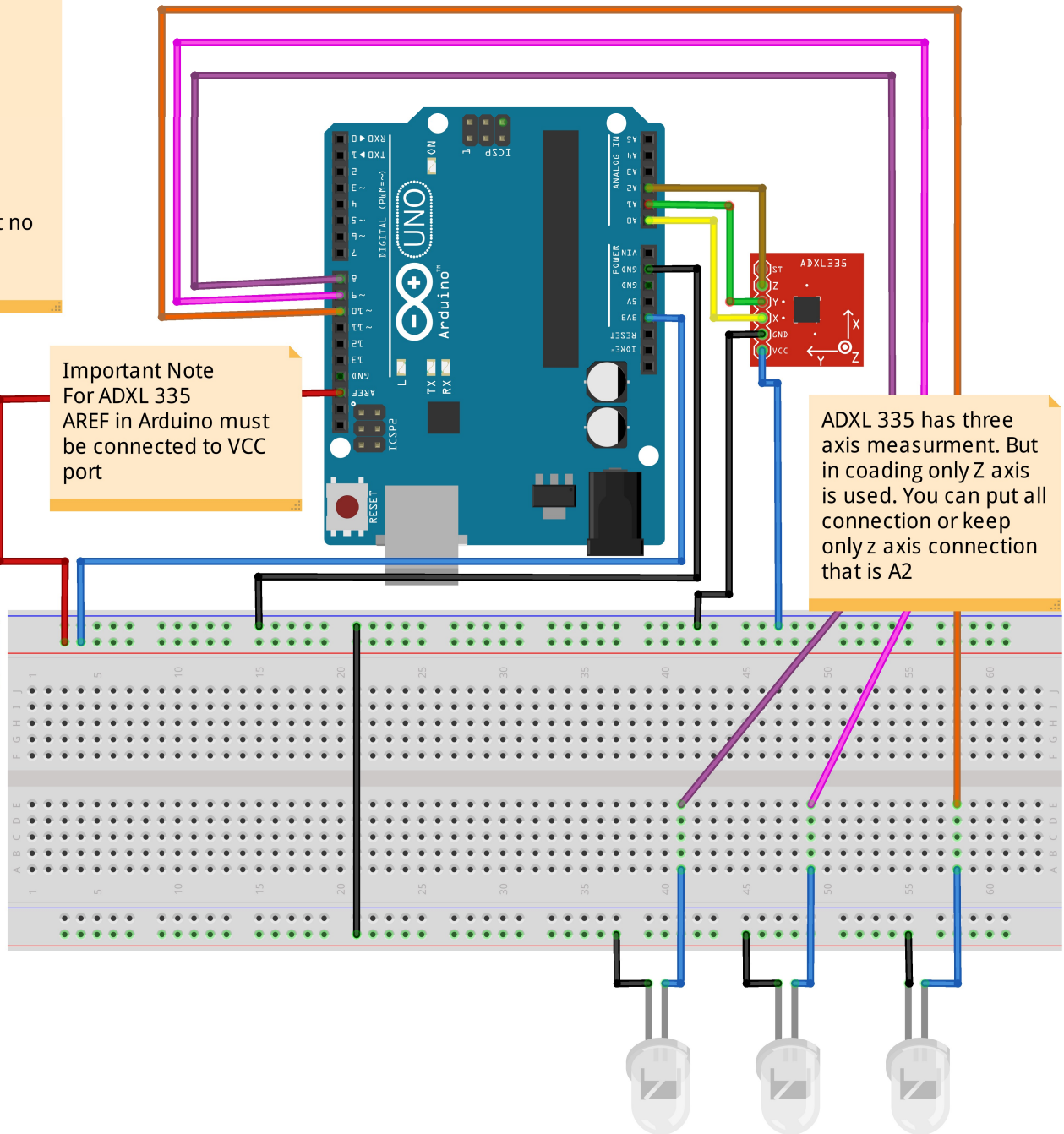

fritzing